


Computer Assignment4

"Multi Cycle Processor"

Ava Mirmohamadmahdi 810199501

Nesa Abbasimoghadam 810199457

DataPath

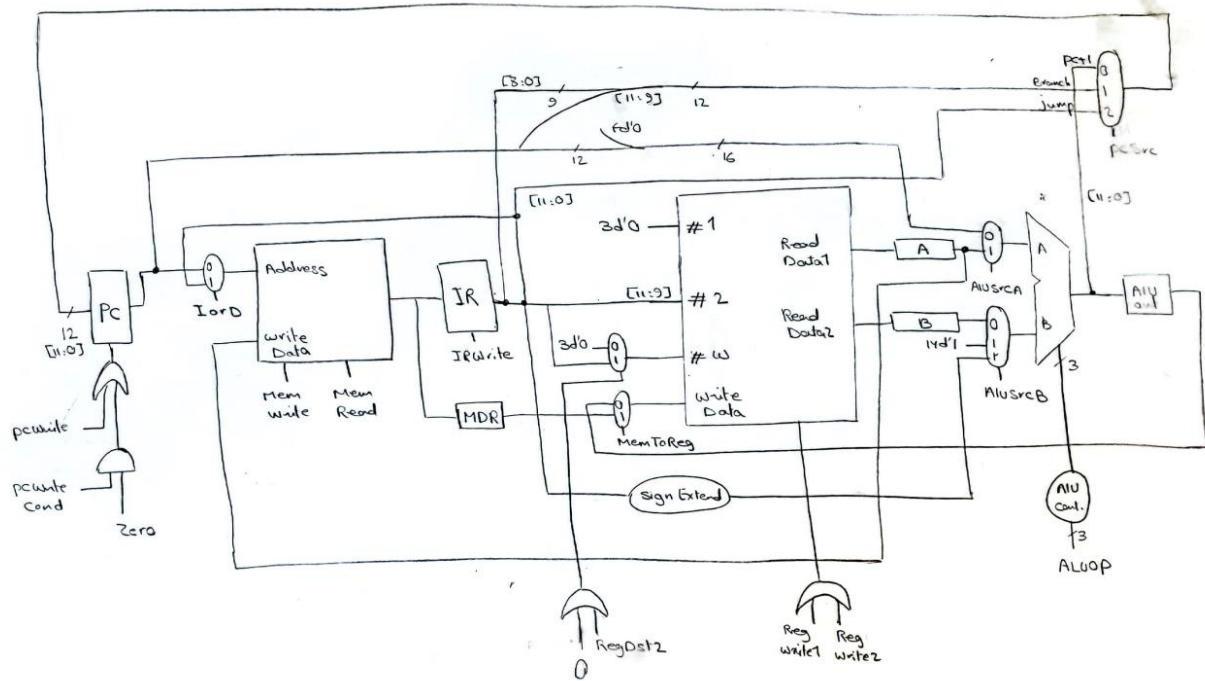

DataPath Verilog

```
module DataPath(memAddress, memWriteData, IROut, zero, memReadData, ALUOperation,
                PCSrc, ALUSrcB, PCLoad, IORD, RegDst, MemToReg, IRWrite, ALUSrcA, RegWrite, clk, rst);
    output [11:0] memAddress;
    output [15:0] memWriteData, IROut;
    output zero;
    input [15:0] memReadData;
    input [2:0] ALUOperation;
    input [1:0] PCSrc, ALUSrcB;
    input PCLoad, IORD, RegDst, MemToReg, IRWrite, ALUSrcA, RegWrite, clk, rst;

    wire [11:0] pcOut;
    wire [11:0] muxPcSrcOut;
    Register #(12) PC(pcOut, muxPcSrcOut, rst, PCLoad, clk);

    wire [11:0] muxIORDOut;
    Mux2To1 #(12) MuxIORD(muxIORDOut, pcOut, IROut[11:0], IORD);

    Register #(16) IR(IROut, memReadData, rst, IRWrite, clk);

    wire [15:0] MDROut;
    Register #(16) MDR(MDROut, memReadData, rst, 1'b1, clk);

    wire [2:0] muxRegDstOut;
    Mux2To1 #(3) MuxRegDst(muxRegDstOut, 3'd0, IROut[11:9], RegDst);

    wire [15:0] ALURegOut;
    wire [15:0] muxMemToRegOut;
    Mux2To1 #(16) MuxMemToReg(muxMemToRegOut, ALURegOut, MDROut, MemToReg);

    wire [15:0] readData1, readData2;
    RegFile RegisterFile(readData1, readData2, muxMemToRegOut, 3'd0, IROut[11:9], muxRegDstOut, RegWrite, rst, clk);

    wire [15:0] signExtend;
    assign signExtend = {{4{IROut[11]}}, IROut[11:0]};

    wire [15:0] RegOutA, RegOutB;
    Register #(16) RegA(RegOutA, readData1, rst, 1'b1, clk);
    Register #(16) RegB(RegOutB, readData2, rst, 1'b1, clk);

    wire [15:0] ALUSrcOutA, ALUSrcOutB;
    wire [15:0] extendedPC;
    assign extendedPC = {4'd0, pcOut};
    Mux2To1 #(16) MuxALUSrcA(ALUSrcOutA, extendedPC, RegOutA, ALUSrcA);
    Mux3To1 #(16) MuxALUSrcB(ALUSrcOutB, RegOutB, 16'd1, signExtend, ALUSrcB);

    wire [15:0] ALUResult;
    ALU ALU(ALUResult, zero, ALUSrcOutA, ALUSrcOutB, ALUOperation);


    Register #(16) RegALU(ALURegOut, ALUResult, rst, 1'b1, clk);

    wire [11:0] extendedBranch;
    assign extendedBranch = {pcOut[11:9], IROut[8:0]};
    Mux3To1 #(12) MuxPCSrc(muxPcSrcOut, ALUResult[11:0], extendedBranch, IROut[11:0], PCSrc);

    assign memAddress= muxIORDOut;
    assign memWriteData = RegOutA;

endmodule
```

Controller

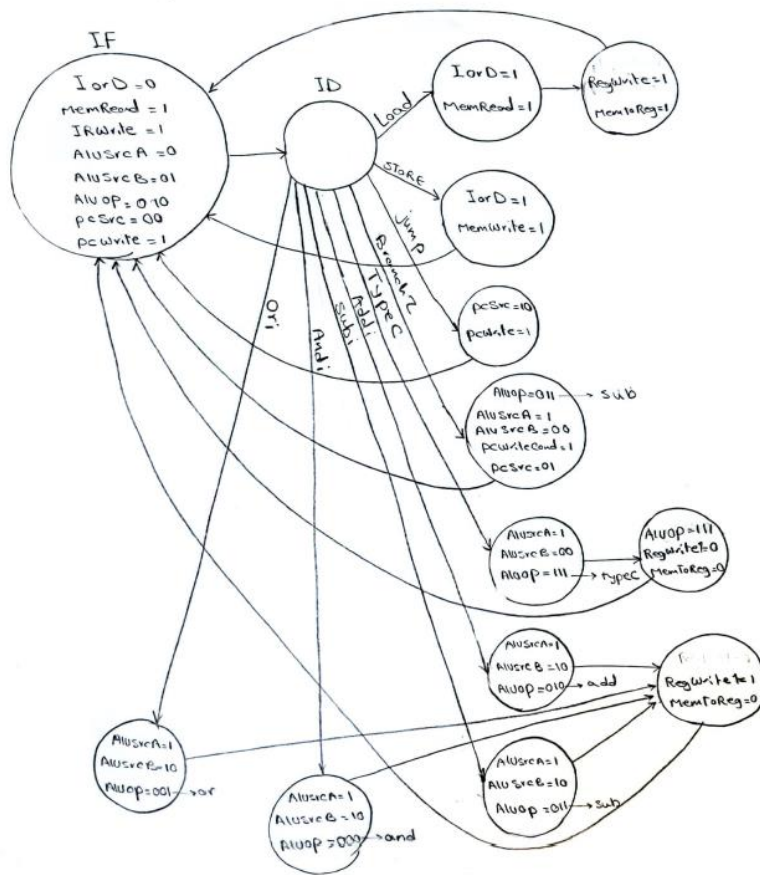

| ALUOP | Func | ALUoperation | Signals |
|-------------|----------|----------------------------|-----------------------|
| 010 | | 010 Add | RegWrite2=0 RegDst2=0 |
| 011 | | 011 Sub | RegWrite2=0 RegDst2=0 |
| 000 | | 000 and | RegWrite2=0 RegDst2=0 |
| 001 | | 001 or | RegWrite2=0 RegDst2=0 |
| 111 (typeC) | 00000001 | 101 not ALUSrcA | RegWrite2=1 RegDst2=1 |
| 111 (typeC) | 00000010 | 100 not ALUSrcB | RegWrite2=1 RegDst2=0 |
| 111 (typeC) | 00000100 | 010 Add | RegWrite2=1 RegDst2=0 |
| 111 (typeC) | 00001000 | 011 Sub | RegWrite2=1 RegDst2=0 |
| 111 (typeC) | 00010000 | 000 and | RegWrite2=1 RegDst2=0 |
| 111 (typeC) | 00100000 | 001 or | RegWrite2=1 RegDst2=0 |
| 111 (typeC) | 01000000 | 110 not LA | RegWrite2=1 RegDst2=0 |
| 111 (typeC) | 10000000 | 111 Nap | RegWrite2=0 |

Controller Verilog

```
always @(ps, opc) begin
  case(ps)
    IF: ns = ID;
    ID: begin
      case(opc)
        LOAD: ns = Load1;
        STORE: ns = Store;
        JUMP: ns = Jump;
        BRANCHZ: ns = BranchZ;
        TYPEC: ns = TypeC1;
        ADDI: ns = Addi;
        SUBI: ns = Subi;
        ANDI: ns = Andi;
        ORI: ns = Ori;
      endcase
    end
    Load1: ns = Load2;
    Load2: ns = IF;
    Store: ns = IF;
    Jump: ns = IF;
    BranchZ: ns = IF;
    TypeC1: ns = TypeC2;
    TypeC2: ns = IF;
    Addi: ns = IState;
    IState: ns = IF;
    Subi: ns = IState;
    Andi: ns = IState;
    Ori: ns = IState;
  endcase
end
```

```

always @(ps) begin
{PCWrite, PCWriteCond, IOrD, MemWrite, MemRead, IRWrite, MemToReg, RegWrite1, ALUSrcB, PCSrc, ALUop, ALUSrcA} = 16'd5;
case(ps)
IF: begin
    IOrD = 1'b0;
    MemRead = 1'b1;
    IRWrite = 1'b1;
    ALUSrcA = 1'b0;
    ALUSrcB = 2'b01;
    ALUop = 3'b010;
    PCSrc = 2'b00;
    PCWrite = 1'b1;
end
ID: begin
    {MemWrite, MemRead, IRWrite, RegWrite1, PCWrite, PCWriteCond} = 6'b000000;
end
Load1: begin
    IOrD = 1'b1;
    MemRead = 1'b1;
end
Load2: begin
    RegWrite1 = 1'b1;
    MemToReg = 1'b1;
end
Store: begin
    IOrD = 1'b1;
    MemWrite = 1'b1;
end
Jump: begin
    PCSrc = 2'b10;
    PCWrite = 1'b1;
end
BranchZ: begin
    ALUop = 3'b011;
    ALUSrcA = 1'b1;
    ALUSrcB = 2'b00;
    PCWriteCond = 1'b1;
    PCSrc = 2'b01;
end
TypeC1: begin
    ALUSrcA = 1'b1;
    ALUSrcB = 2'b00;
    ALUop = 3'b111;
end
TypeC2: begin
    ALUop = 3'b111;
    RegWrite1 = 1'b0;
    MemToReg = 1'b0;
end
Addi: begin
    ALUSrcA = 1'b1;
    ALUSrcB = 2'b10;
    ALUop = 3'b010;
end
IState: begin
    RegWrite1 = 1'b1;
    MemToReg = 1'b0;
end
Subi: begin
    ALUSrcA = 1'b1;
    ALUSrcB = 2'b10;
    ALUop = 3'b011;
end
Andi: begin
    ALUSrcA = 1'b1;
    ALUSrcB = 2'b10;
    ALUop = 3'b000;
end
Ori: begin
    ALUSrcA = 1'b1;
    ALUSrcB = 2'b10;
    ALUop = 3'b001;
end
endcase
end

```

Instructions

```
andi 0          # R0 = 0
ori 2047         # R0 = 2047
add 0           # R0 = 4094
add 0           # R0 = 8188
add 0           # R0 = 16376
add 0           # R0 = 32752
addi 16         # R0 = 32768
mvto 4          # R4 = 0x8000
andi 0          # R0 = 0
mvto 5          # R5 = 0

mvto 6          # R6 = 0 maxIndex
load 100        # R0 = mem[100]
mvto 7          # R7 = mem[100] -> max

load 101        # R0 = mem[101]
mvto 2          # R2 = mem[101] -> temp
sub 7           # R0 = temp - max
and 4           # R0 & 0x8000
branch 5, 239   # R0 == 0
jump 244

mvfrom 2        # R0 = temp
mvto 7          # max = temp
andi 0          # R0 = 0
ori 01          # R0 = 1
mvto 6          # R6 = 1 maxIndex
```



20 Random Numbers

```
0: 546      1: -87
2: 0        3: 178
4: 13       5: -23
6: 764      7: 15
8: 369      9: -783
10: -1      11: 3
12: 125     13: 93
14: -263    15: -7
16: 37      17: 88
18: 20      19: -1
```



| | | | |
|---------------------|-----|-----|--|
| /TestBench/max | 764 | 764 | |
| /TestBench/maxIndex | 6 | 6 | |

Waveforms

  

مقدار بزرگترین عنصر در خانه ۲۰۰ ذخیره شده است.

اندیس بزرگترین عنصر در خانه ۲۰۴ ذخیره شده است.