


Computer Assignment2

"Single Cycle MIPS Processor"

Ava Mirmohamadmahdi 810199501

Nesa Abbasimoghdam 810199457

DataPath:

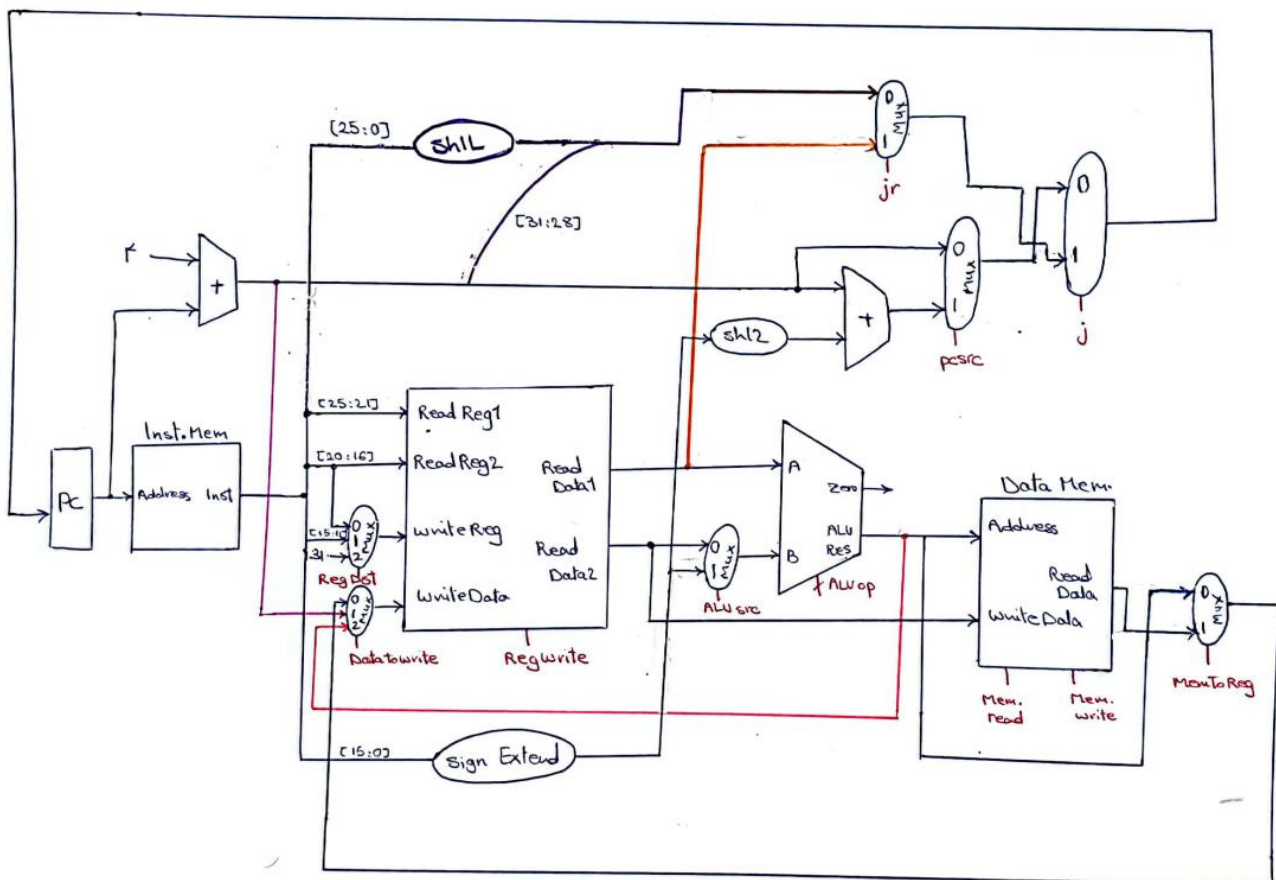

```

module DataPath(instMemAddress, dataMemAddress, dataMemWriteData, zero, instruction, dataMemReadData, ALUOperation,
                RegDst, DataToWrite, MemToReg, ALUSrc, PCSrc, RegWrite, Jr, J, clk, rst);
output [31:0] instMemAddress, dataMemAddress, dataMemWriteData;
output zero;
input [31:0] instruction, dataMemReadData;
input [2:0] ALUOperation;
input [1:0] RegDst, DataToWrite;
input MemToReg, ALUSrc, PCSrc, RegWrite, Jr, J, clk, rst;

wire [31:0] pcOut;
wire [31:0] muxJOut;
Reg32Bit PC(pcOut, muxJOut, rst, 1'b1, clk);

wire [31:0] adderPcOut;
Adder32Bit AdderPc(adderPcOut, pcOut, 32'd4);

wire [4:0] muxRegDstOut;
Mux3To1 #(5) MuxRegDst(muxRegDstOut, instruction[20:16], instruction[15:11], 5'd31, RegDst);

wire [31:0] muxDataToWriteOut;
wire [31:0] ALUResult;
wire [31:0] muxMemToRegOut;
Mux3To1 #(32) MuxDataToWrite(muxDataToWriteOut, muxMemToRegOut, adderPcOut, ALUResult, DataToWrite);

wire [31:0] readData1, readData2;
RegFile RegisterFile(readData1, readData2, muxDataToWriteOut, instruction[25:21], instruction[20:16], muxRegDstOut, RegWrite, rst, clk);

wire [31:0] signExtend;
assign signExtend = {{16{instruction[15]}}, instruction[15:0]};

wire [31:0] ALUSrcOut;
Mux2To1 #(32) MuxALUSrc(ALUSrcOut, readData2, signExtend, ALUSrc);

ALU Alu(ALUResult, zero, readData1, ALUSrcOut, ALUOperation);

wire [31:0] shift2Beq;
wire [31:0] adderBeqOut;
assign shift2Beq = signExtend << 2;
Adder32Bit AdderBeq(adderBeqOut, adderPcOut, shift2Beq);

wire [31:0] muxPCSrcOut;
Mux2To1 #(32) MuxPCSrc(muxPCSrcOut, adderPcOut, adderBeqOut, PCSrc);

wire [27:0] shiftJOut;
wire [31:0] jOut;
assign shiftJOut = {instruction[25:0], 2'b00};
assign jOut = {adderPcOut[31:28], shiftJOut};

wire [31:0] muxJrOut;
Mux2To1 #(32) MuxJr(muxJrOut, jOut, readData1, Jr);

Mux2To1 #(32) MuxJ(muxJOut, muxPCSrcOut, muxJrOut, J);

Mux2To1 #(32) MuxMemToReg(muxMemToRegOut, ALUResult, dataMemReadData, MemToReg);

assign instMemAddress= pcOut;
assign dataMemAddress = ALUResult;
assign dataMemWriteData = readData2;

endmodule

```

Controller:

	RegDst	ALUSrc	Mem to Reg	Reg write	Mem Read	Mem write	pcsrc	ALU Operation	J	Jr	Data to write
add	01	0	1	1	—	0	0	010	0	—	00
sub	01	0	1	1	—	0	0	011	0	—	00
and	01	0	1	1	—	0	0	000	0	—	00
or	01	0	1	1	—	0	0	001	0	—	00
sll	01	0	1	1	—	1	0	111	0	—	00
slli	00	1	—	1	—	0	0	111	0	—	10
lw	00	1	1	1	1	0	0	010	0	—	00
sw	—	1	1	0	—	1	0	010	0	—	—
beq	—	0	—	0	—	0	don't know	011	0	—	—
j	—	—	—	0	—	0	0	—	1	0	—
jal	10	—	—	1	—	0	0	—	1	0	01
jr	—	—	—	0	—	0	0	—	1	1	—
addi	00	1	0	1	—	0	0	010	0	—	00

```

module AluController(ALUoperation, ALUop, func);
    output reg [2:0] ALUoperation;
    input [1:0] ALUop;
    input [5:0] func;
    parameter [5:0] And = 6'b100100, Or = 6'b100101, Add = 6'b100000, Sub = 6'b100010, Slt = 6'b101010;
    always@(ALUop, func) begin
        ALUoperation = 3'b010;
        if(ALUop == 2'd0) // lw or sw
            ALUoperation = 3'b010;
        else if(ALUop == 2'd1) // beq
            ALUoperation = 3'b011;
        else if(ALUop == 2'd2) begin
            case(func)
                And: ALUoperation = 3'b000;
                Or: ALUoperation = 3'b001;
                Add: ALUoperation = 3'b010;
                Sub: ALUoperation = 3'b011;
                Slt: ALUoperation = 3'b111; // slt & slti
                default: ALUoperation = 3'b000;
            endcase
        end
        else
            ALUoperation = 3'b111;
        end
    end
endmodule

```

```

parameter [5:0] RType = 6'b000000, Lw = 6'b100011, Sw = 6'b101011, Beq = 6'b000100, Addi = 6'b001000,
Jump = 6'b000010, Jal = 6'b000011, JumpR = 6'b000110, Slti = 6'b001010;

always @(opc)begin
{RegDst, ALUSrc, MemToReg, RegWrite, MemRead, MemWrite, branch, ALUop, J, Jr, DataToWrite} = 14'd0;
case (opc)
RType : begin
    RegDst = 2'b01;
    RegWrite = 1'b1;
    ALUop = 2'b10;
end

Addi: begin
    RegWrite = 1'b1;
    ALUSrc = 1'b1;
end

Sw : begin
    ALUSrc = 1'b1;
    MemWrite = 1'b1;
end

Lw : begin
    ALUSrc = 1'b1;
    MemToReg = 1'b1;
    RegWrite = 1'b1;
    MemRead = 1'b1;
end

Jump: begin
    J = 1'b1;
end

JumpR: begin
    Jr = 1'b1;
    J = 1'b1;
end


Jal: begin
    RegDst = 2'b10;
    DataToWrite = 2'b01;
    J = 1'b1;
end

Beq : begin
    branch = 1'b1;
    ALUop = 2'b01;
end


Slti: begin
    RegWrite = 1'b1;
    ALUSrc = 1'b1;
    ALUop = 2'b11;
    DataToWrite = 2'b10;
end
endcase
end
assign PCSrc = branch & zero;

```


Instruction Formats:

 


addi

 


j

 


jal

 


jr

 


slti

 

lw/sw

 

beq

 

Cpp code – Find Max Numebr:

```
int main() {
    int arr[20];
    int max = arr[0];
    for (int i = 1; i < 20; i++) {
        if (arr[i] > max) {
            max = arr[i];
        }
    }
    return max;
}
```

Assembly Instructions:

```

                LW    R1, 1000(R0)
                ADDI  R2, R1, 0
                ADDI  R3, R0, 1
                ADDI  R8, R0, 0
                ADDI  R4, R0, 20
loop:           BEQ   R3, R4, afterLoop
                ADD   R5, R0, 0
                ADD   R5, R5, R5
                ADD   R5, R5, R5
                LW    R6, 1000(R5)
                SLT   R7, R2, R6
                BEQ   R7, R0, endLoop
                ADD   R2, R6, R0
                ADD   R8, R3, R0
endLoop:       ADDI  R3, R3, 1
                J     loop
afterLoop:     SW    R2, 2000(R0)
                SW    R8, 2004(R0)
```

20 random numbers:

0: 158	1: 754
2: -346	3: 3
4: 53	5: 77
6: 1500	7: -1780
8: 237	9: -17
10: 149	11: 82
12: 456	13: 4573
14: -2000	15: 3324
16: 85	17: 10
18: 3452	19: -56

/TestBench/max	4573	4573
/TestBench/maxIndex	13	13

